
 



MIPS-4712 General Architecture

 


Deliverable 1: MIPS ALU



Deliverable 2: MIPS-4712 Memory/Port Module

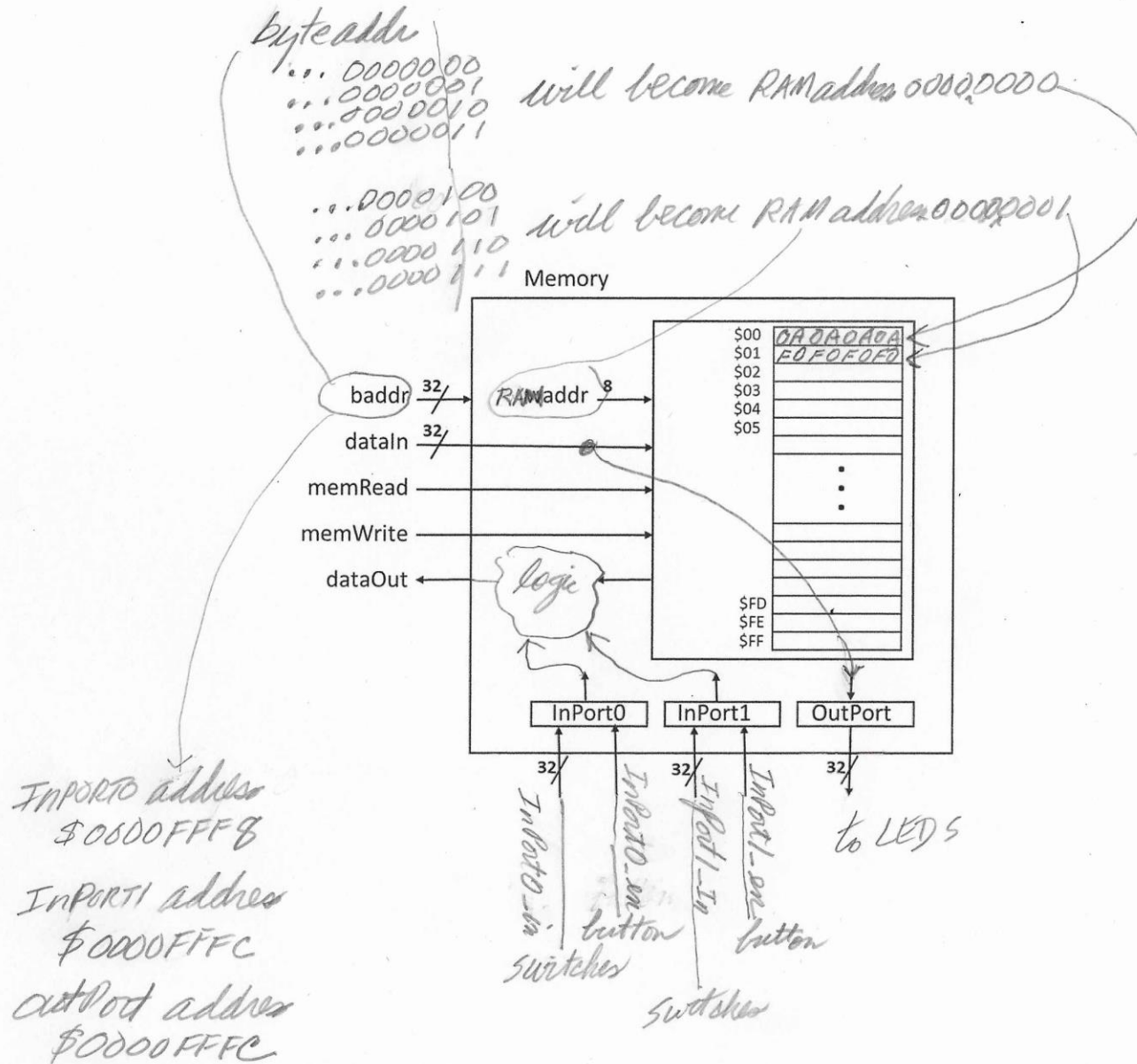


Deliverable 3: Datapath

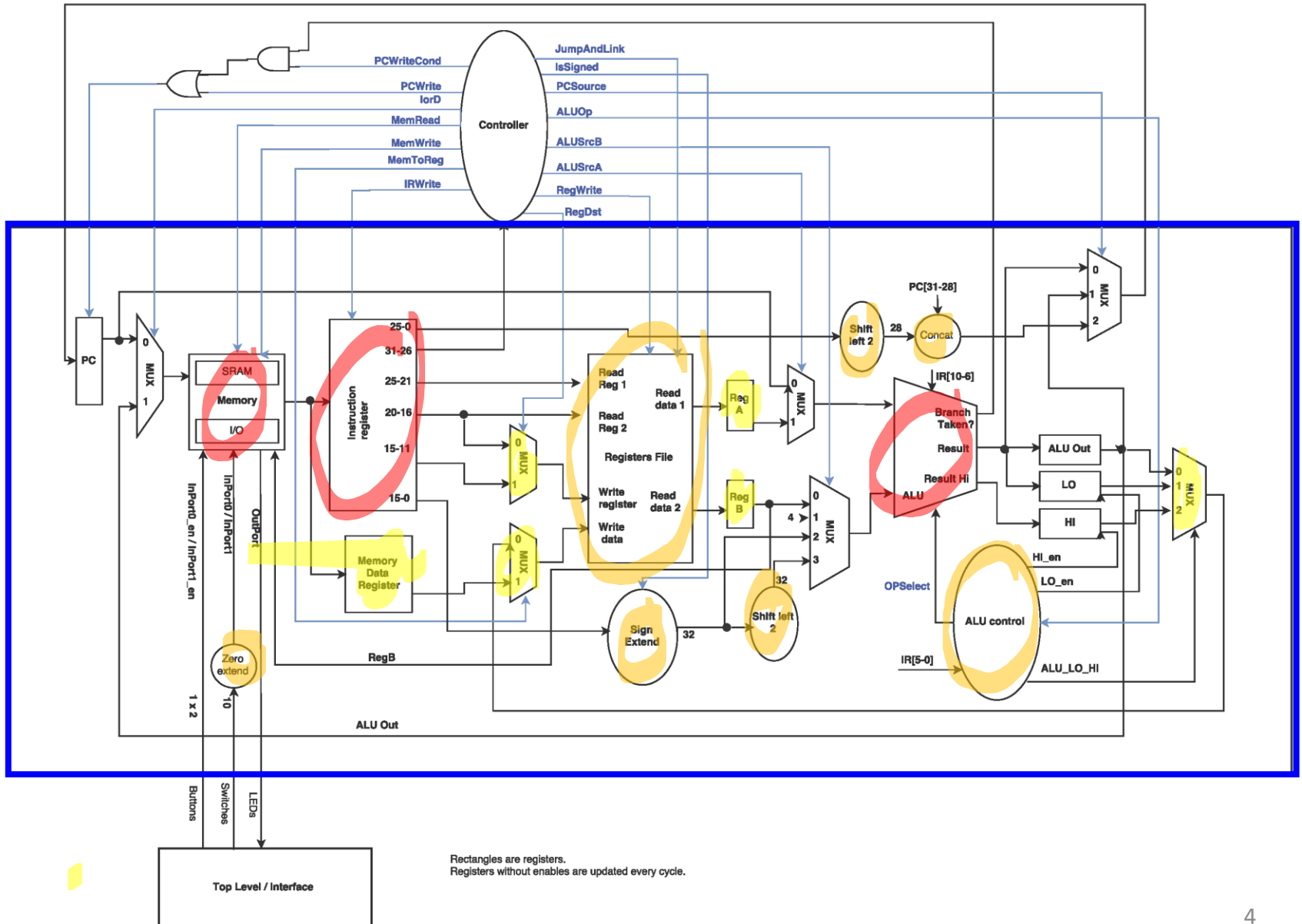

MIPS-4712 Register File

registerfile

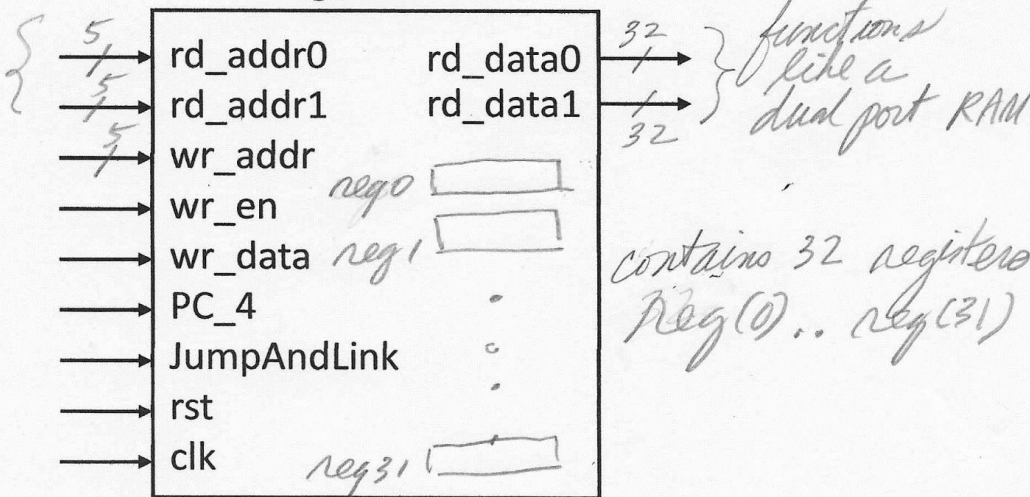

Number	Name	Comments
\$0	\$zero, \$r0	Always zero
\$1	\$at	Reserved for assembler
\$2, \$3	\$v0, \$v1	First and second return values, respectively
\$4, ..., \$7	\$a0, ..., \$a3	First four arguments to functions
\$8, ..., \$15	\$t0, ..., \$t7	Temporary registers
\$16, ..., \$23	\$s0, ..., \$s7	Saved registers
\$24, \$25	\$t8, \$t9	More temporary registers
\$26, \$27	\$k0, \$k1	Reserved for kernel (operating system)
\$28	\$gp	Global pointer
\$29	\$sp	Stack pointer
\$30	\$fp	Frame pointer
\$31	\$ra	Return address

- **Name** is the symbolic name used in the MIPS assembly language instruction.
- **Number** is the actual register number.

Example:

`addu $s3, $s1, $s2`

means $(\text{reg}19) = (\text{reg}17) + (\text{reg}18)$

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity registerfile is
  port(
    clk : in std_logic;
    rst : in std_logic;

    rd_addr0 : in std_logic_vector(4 downto 0); --read reg 1
    rd_addr1 : in std_logic_vector(4 downto 0); --read reg 2

    wr_addr : in std_logic_vector(4 downto 0); --write register
    wr_en : in std_logic;
    wr_data : in std_logic_vector(31 downto 0); --write data

    rd_data0 : out std_logic_vector(31 downto 0); --read data 1
    rd_data1 : out std_logic_vector(31 downto 0); --read data 2
    --JAL
    PC_4 : in std_logic_vector(31 downto 0);
    JumpAndLink : in std_logic
  );
end registerfile;

```

architecture sync_read of registerfile is

type reg_array is array(0 to 31) of std_logic_vector(31 downto 0);

signal regs : reg_array;

begin

process (clk, rst) is

begin

if (rst = '1') then

for i in regs'range loop

regs(i) <= (others => '0');

end loop;

elsif (rising_edge(clk)) then

if (wr_en = '1') then

regs(to_integer(unsigned(wr_addr))) <= wr_data;

regs(0) <= (others => '0');

end if;

if(JumpAndLink = '1') then

regs(31) <= PC_4;

end if;

rd_data0 <= regs(to_integer(unsigned(rd_addr0)));


rd_data1 <= regs(to_integer(unsigned(rd_addr1)));

end if;

end process;

end sync_read;

Deliverable 3: Datapath

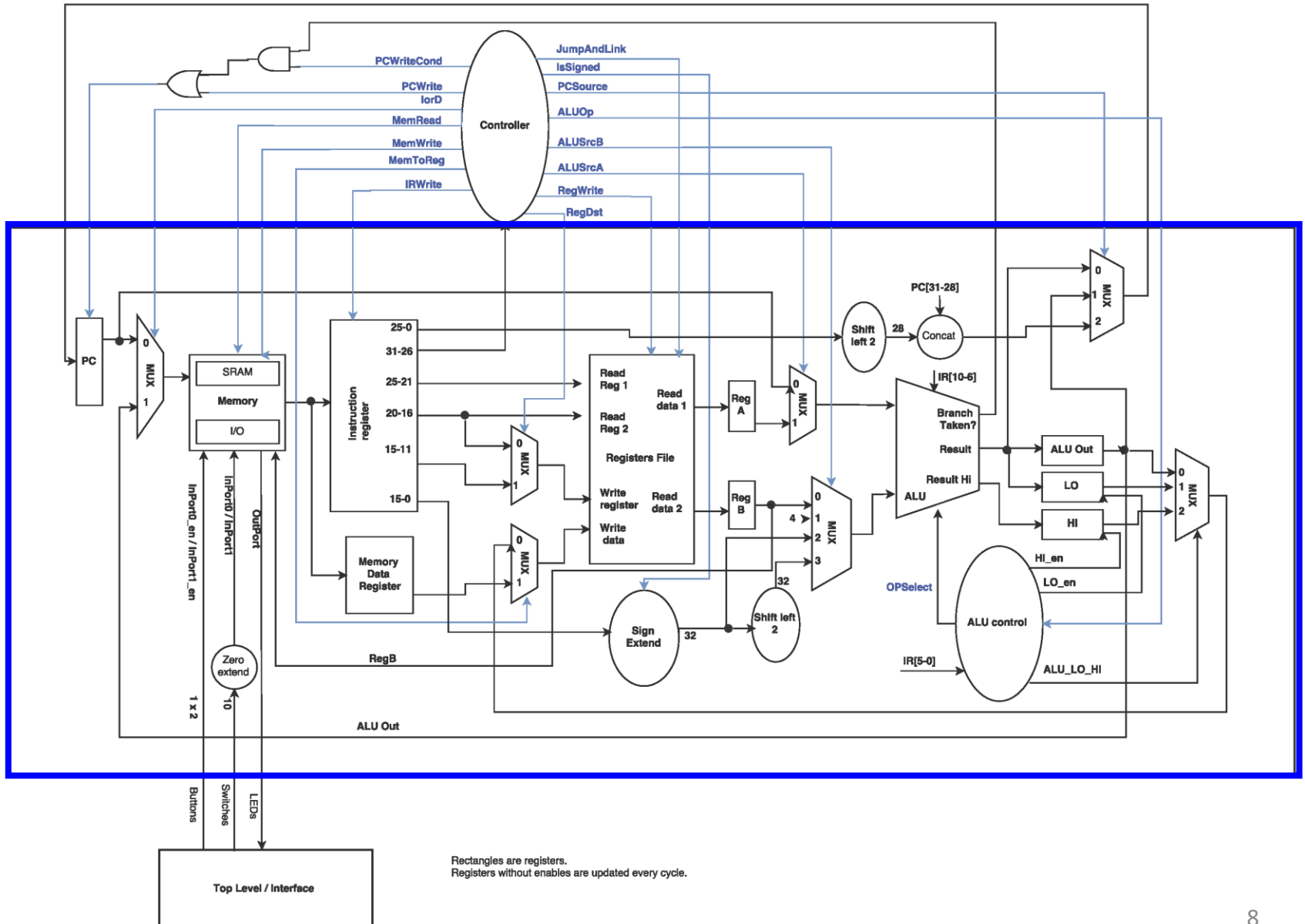

Deliverable 3: RTL View of Datapath


 


Figure 3. General algorithm for designing a controller for a MIPS CPU

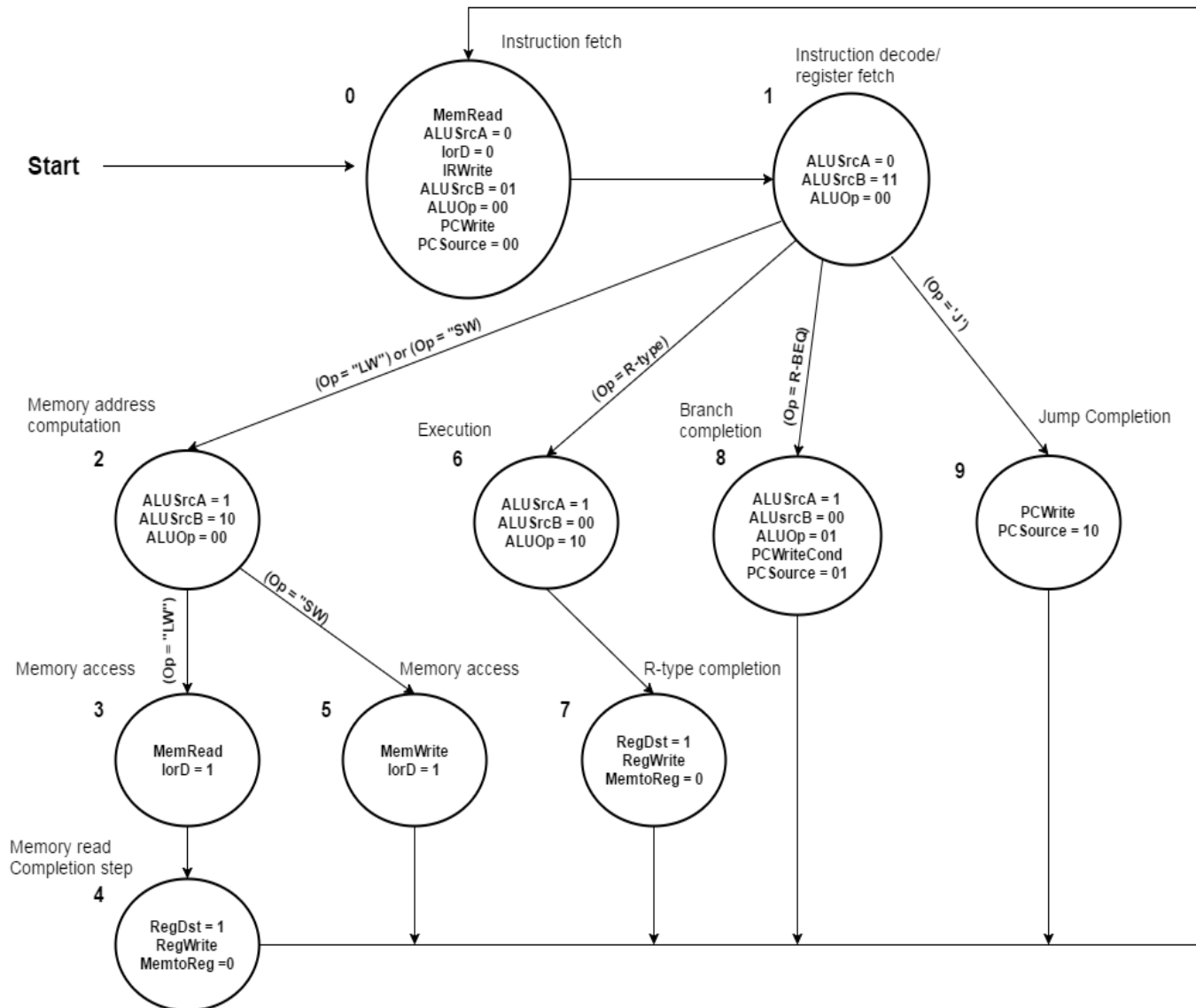Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed



General "ASM Chart" for Controller

 


Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed


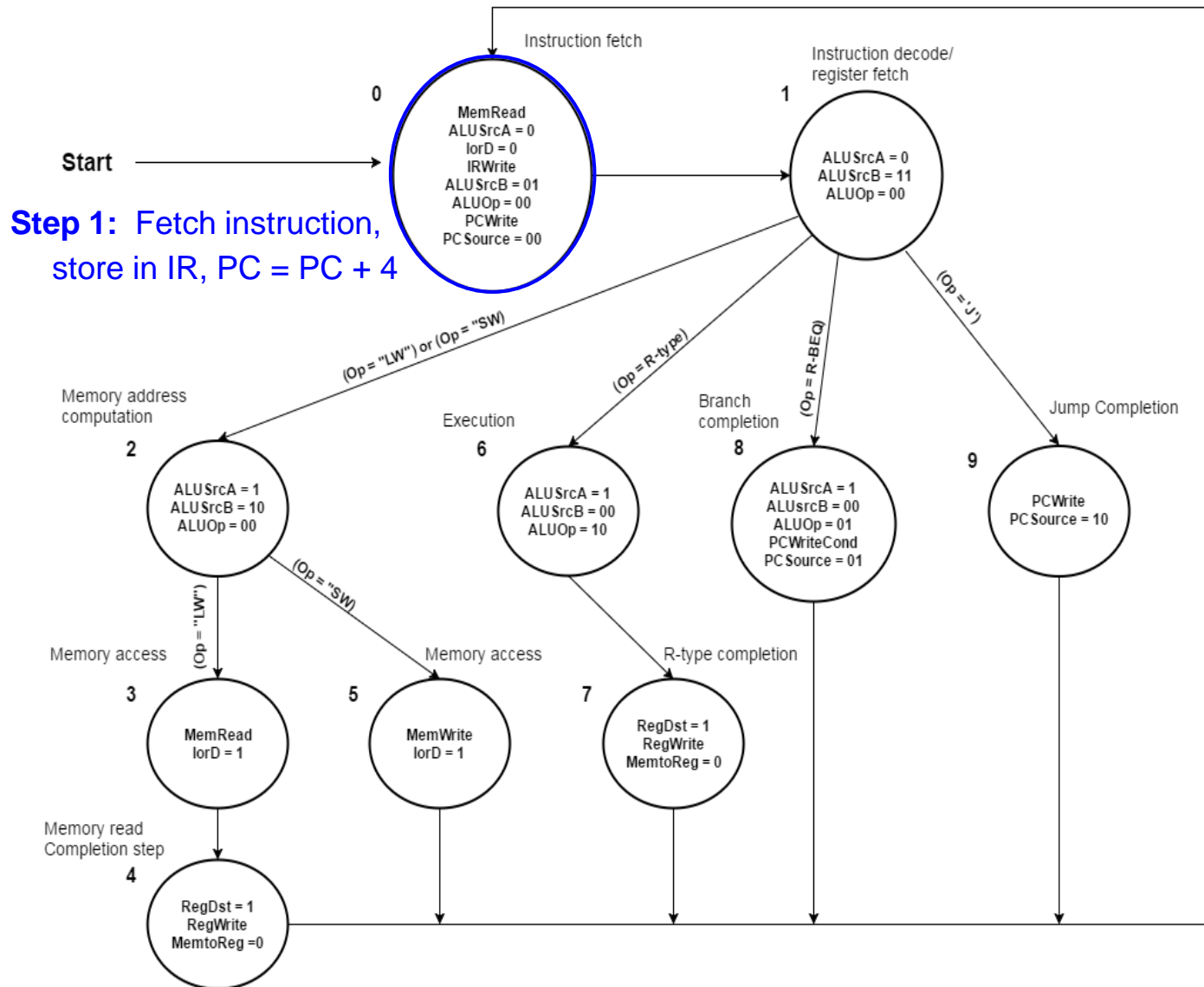


Illustration of the Instruction Fetch State

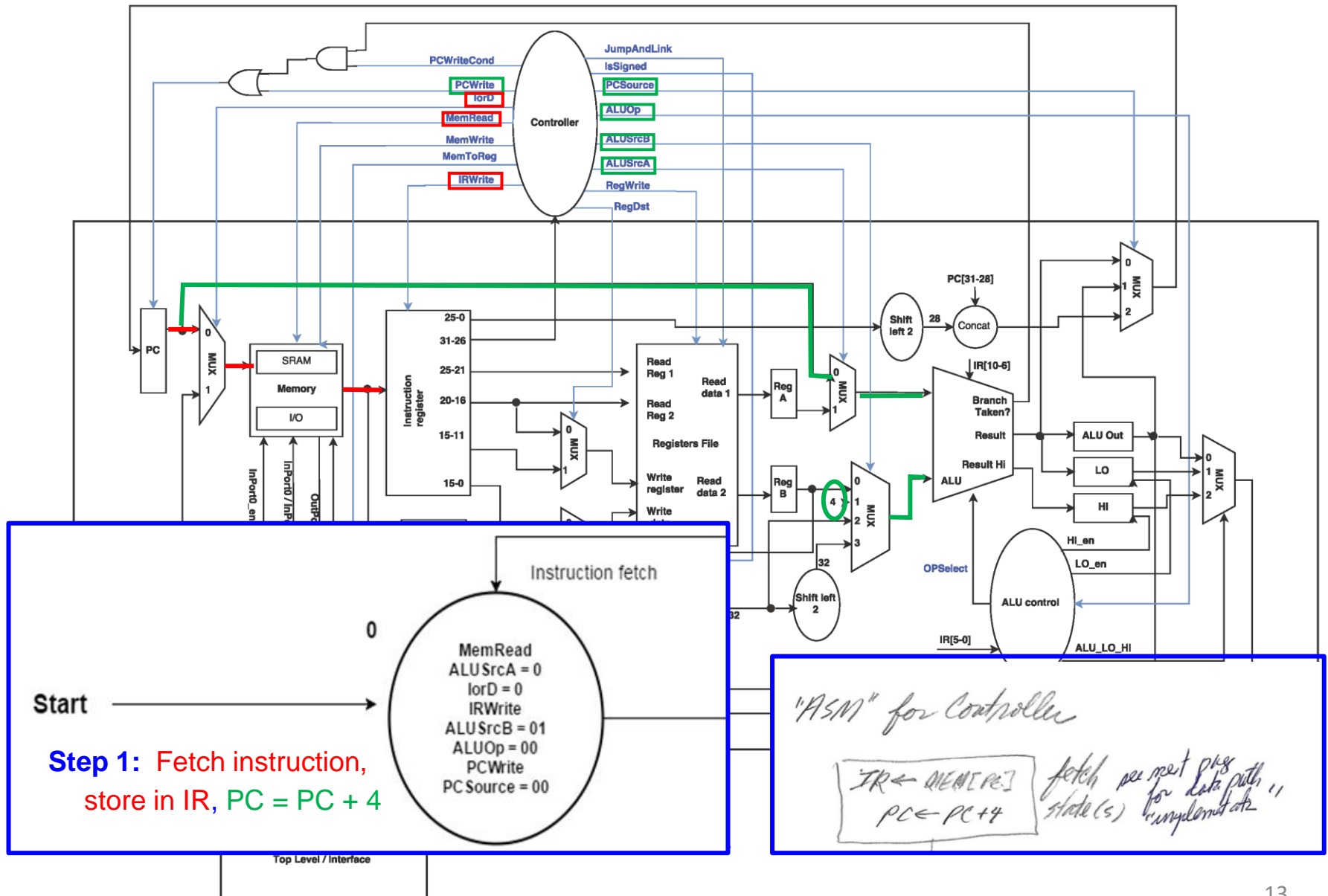

R-Type Instruction Format

31-26	25-21	20-16	15-11	10-6	5-0
<i>opcode</i> (000000)	<i>rs</i>	<i>rt</i>	<i>rd</i>	<i>shamt</i>	<i>funct</i>

- ***rs*** and ***rt*** are operand registers; ***rd*** is the destination register.
- **R-Type**: Register-based ALU operations.
- ***opcode*** is always 000000.
- The actual instruction code is in the ***funct*** field (5-0).
- ***shamt*** is the “shift amount” for shift instructions.
- MIPS-4712 R-type instructions: (See MIPS instruction Set Manual for details):
add, addu, and, mfhi, mflo, mult, multu, or, sll, sltu, sra, srl, sub, subu, xor
- Example: `and $s4, $s2, $s3` (`s4 = s2 and s3`) or (`reg20 = reg18 and reg19`)
000000 10010 10011 10100 00000 100100

I-Type Instruction Format (ALU immediate)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>immed.</i>

- ***rs*** is operand A register and ***rt*** is destination register.
- ***immed.*** is operand B.
- MIPS-4712 I-type ALU insts.: *addiu, andi, ori, “subiu” (does not exist), xori*
- Example: `addiu $s2, $s1, 7` (`s2 = s1 + 7`) or (`reg18 = reg17 + 7`)
001100 10011 01010 000000000000111

I-Type Instruction Format (Load or Store)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>address</i>

- ***rs***: address base register; ***rt***: source (store) or destination (load) location in register file; ***address***: offset address
- MIPS-4712 I-type load/store instructions: **lw**, **sw**
- Example: **lw \$s2, 0xA(\$Zero)** 100011 00000 10010 0000000000**101000**

I-Type Instruction Format (Branch)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>address</i>

- ***rs***: operand A for conditional branch; ***rt***: operand B for conditional branch; ***address***: offset address for branch (+ or – locations relative to next inst.)
- MIPS-4712 I-type branch instructions: **beq**, **bne**, **jr**
- Example: **beq \$s2 , \$zero, 8** 000100 10010 00000 0000000000000000**11**
(assumption: This beq instruction is in Location 4.)

J-Type Instruction Format (Jump)

31-26	25-0
<i>opcode</i>	<i>target</i>

- ***target***: destination location for jump operation
- MIPS-4712 J-type instructions: **j**, **jal**
- Example: **j8** 000010 000000000000000000000000**1000**

Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed


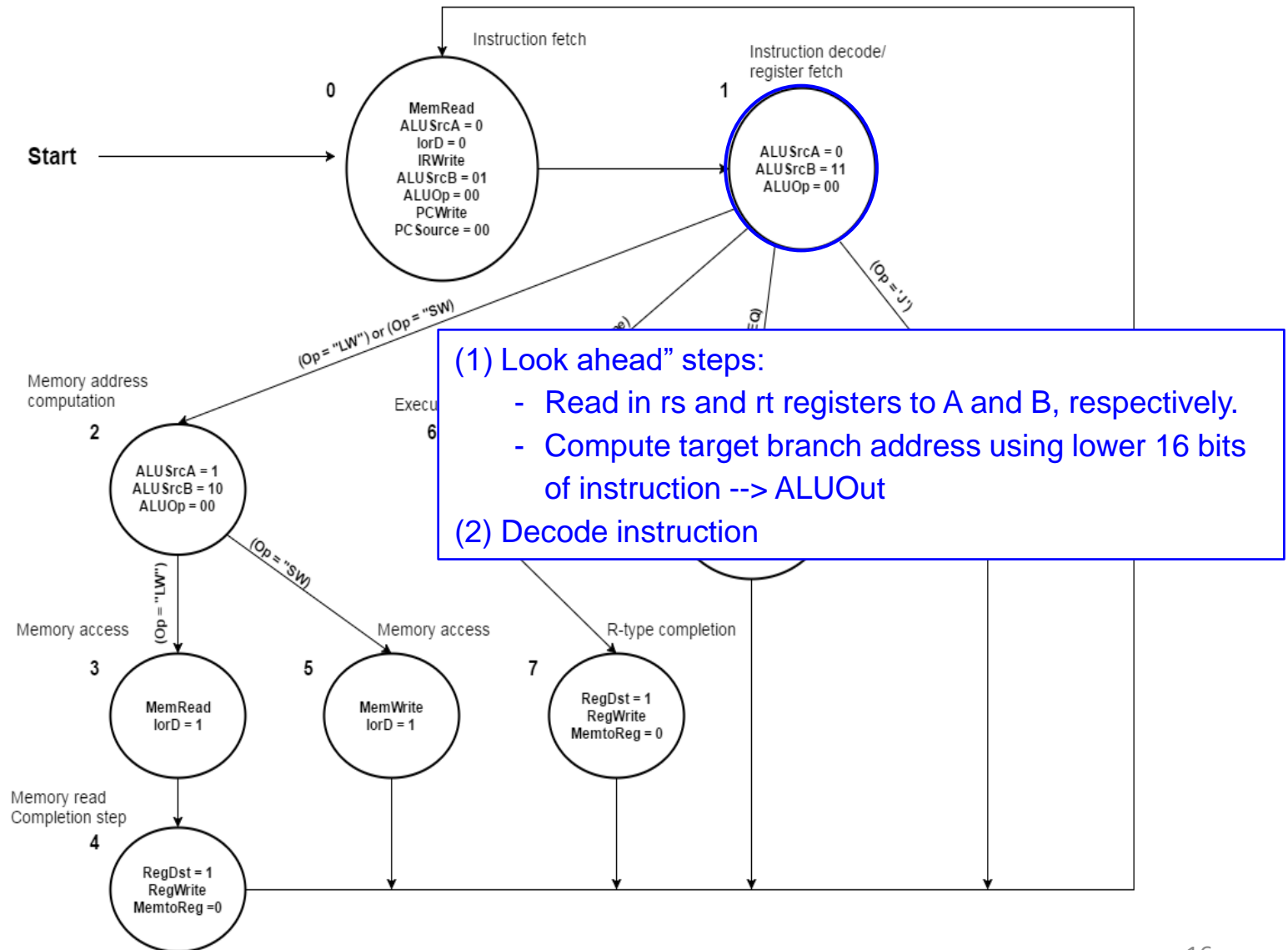


Illustration of the Decode/Register Fetch State

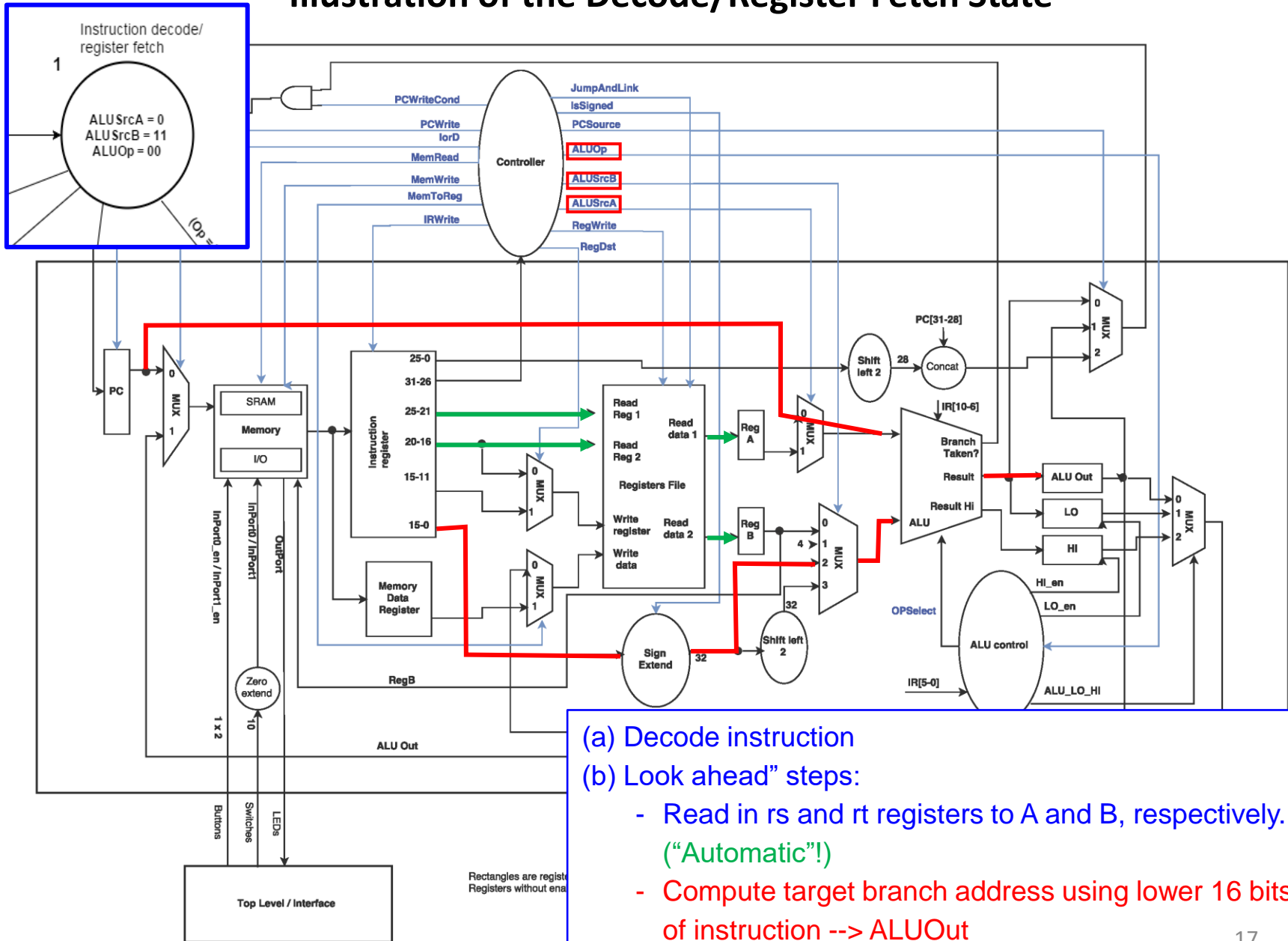

R-Type Instruction Format

31-26	25-21	20-16	15-11	10-6	5-0
<i>opcode</i> (000000)	<i>rs</i>	<i>rt</i>	<i>rd</i>	<i>shamt</i>	<i>funct</i>

I-Type Instruction Format (ALU immediate)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>immed.</i>

I-Type Instruction Format (Load or Store)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>address</i>

I-Type Instruction Format (Branch)


31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>address</i>

J-Type Instruction Format (Jump)


31-26	25-0
<i>opcode</i>	<i>target</i>

Figure 3. General algorithm for designing a controller for a MIPS CPU

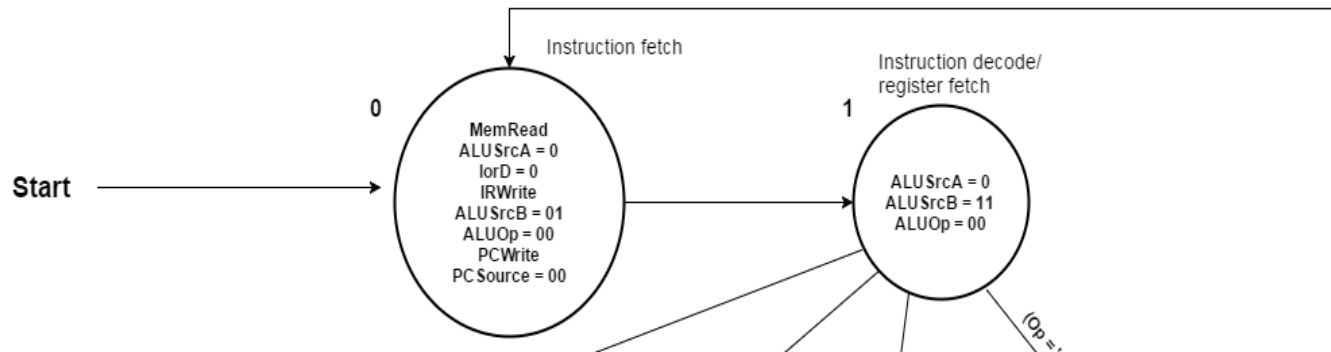Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed



lw and **sw** Instructions

 

Memory access instructions:


2: Compute memory address

3: lw only: Retrieve data from memory at specified address and place in MDR

4: lw only: Write contents of MDR to specified register

5: sw only: Write data (B register) to memory at specified address

Illustration of the lw and sw Instructions

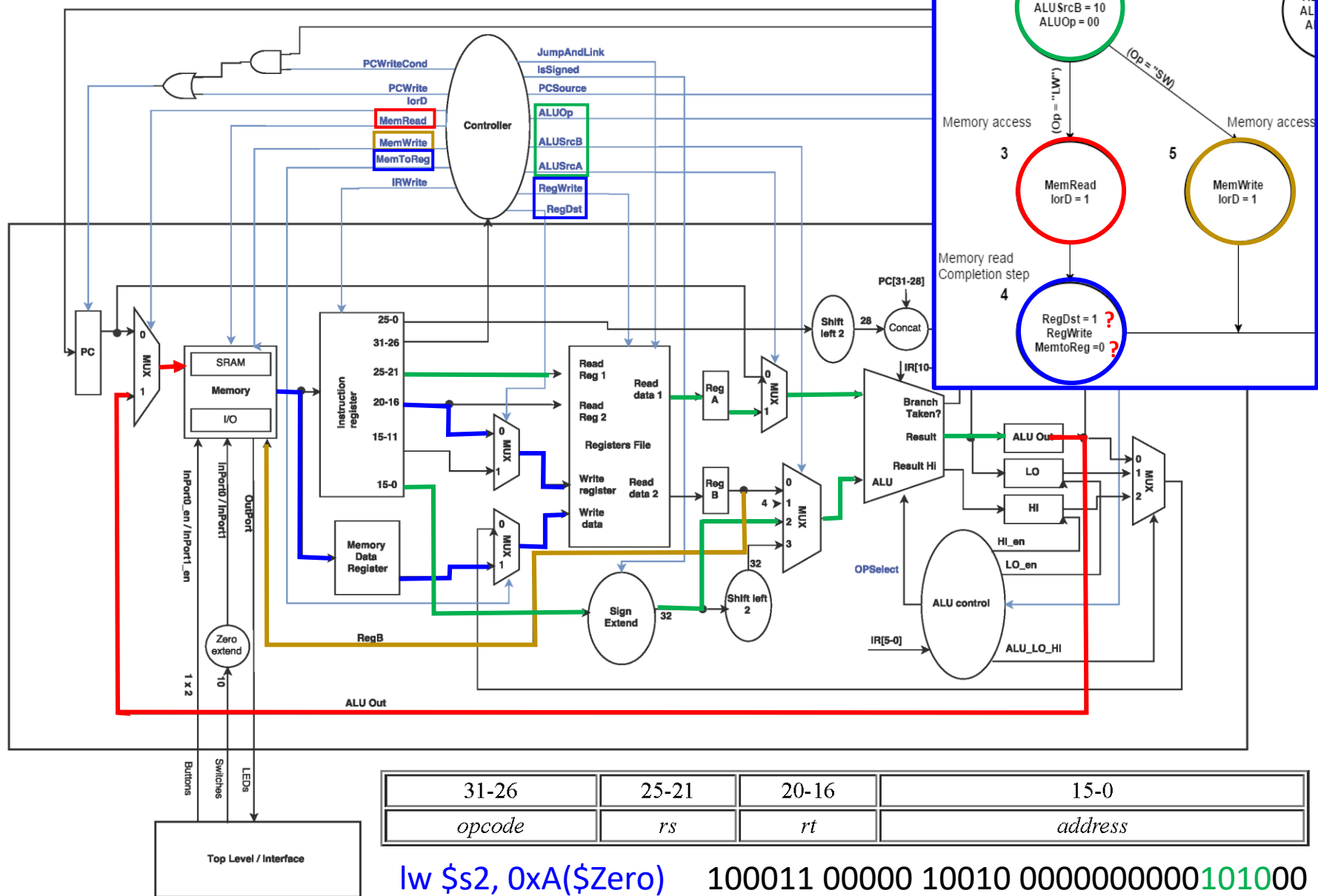

TestCase1.mif

```
% Program RAM Data %      -- This program will test these instructions :
                             -- lw, addu, and, xor, or, sub, multu, and j
00 : 100011000001000100000000000100100;      -- lw $s1, 0x9($Zero)
        /      load word in adress 0x9 + zero to s1      // s1/r17 = 4
01 : 100011000001001000000000000101000;      -- lw $s2, 0xA($zero)
        /      load word in adress 0xA // s2/r18 = 5
02 : 000000100011001010011000000100001;      -- addu $s3, $s1, $s2
        /      s3 = s1 + s2      // s3/r19 = 9
03 : 00000010010100111010000000100100;      -- and $s4, $s2, $s3
        /      s4 = s2 and s3      // s4/r20 = 1
04 : 00000010011101001010100000100110;      -- xor $s5, $s3, $s4
        /      s5 = s3 xor s4      // s5/r21 = 8
05 : 00000010011100011011000000100101;      -- or $s6, $s3, $s1
        /      s6 = s3 or s1      // s6/r22 = D
06 : 00000010110101001011100000100011;      -- sub $s7, $s6, $s4
        /      s7 = s6 - s4      // s7/r23 = C
07 : 00000010011100100000000000011001;      -- multu $s3, $s2
        /      Lo = s3 * s2      // LO = 2D
08 : 00001000000000000000000000000001000;      -- j 8      / infinite loop
09 : 000000000000000000000000000000000100;      -- 4
0A : 000000000000000000000000000000000101;      -- 5
```

Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed

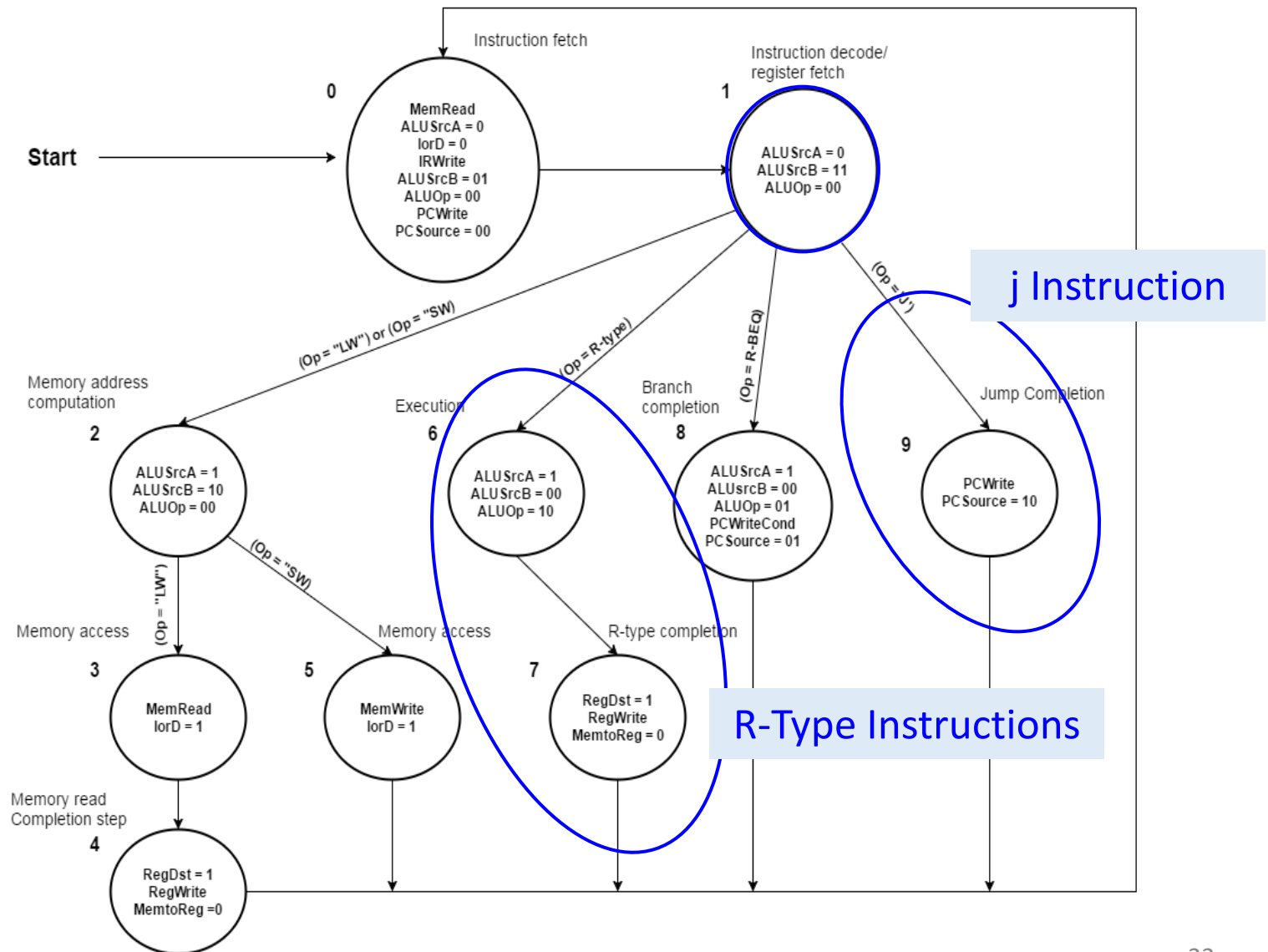


Illustration of j instruction


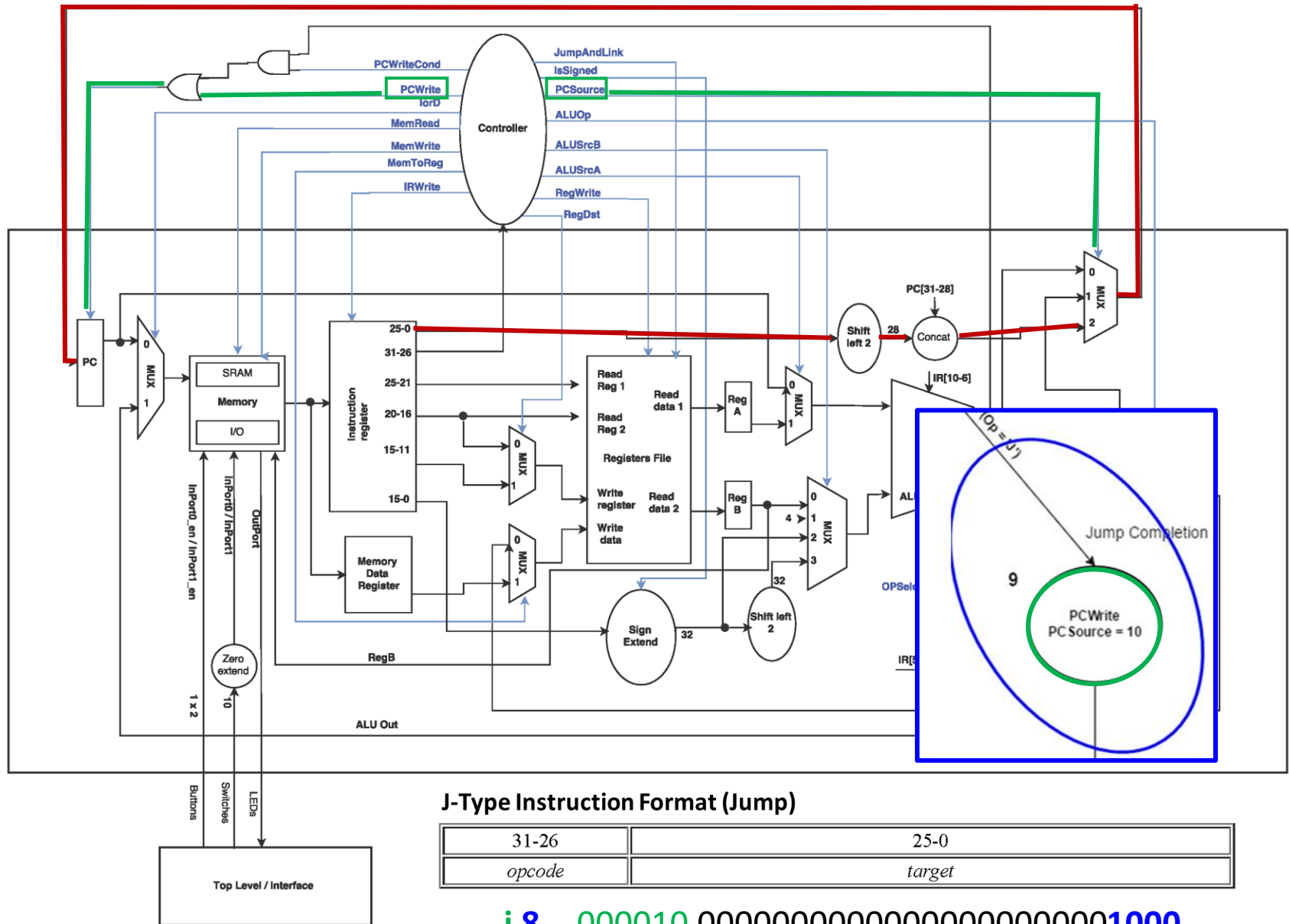


Figure 3. General algorithm for designing a controller for a MIPS CPU

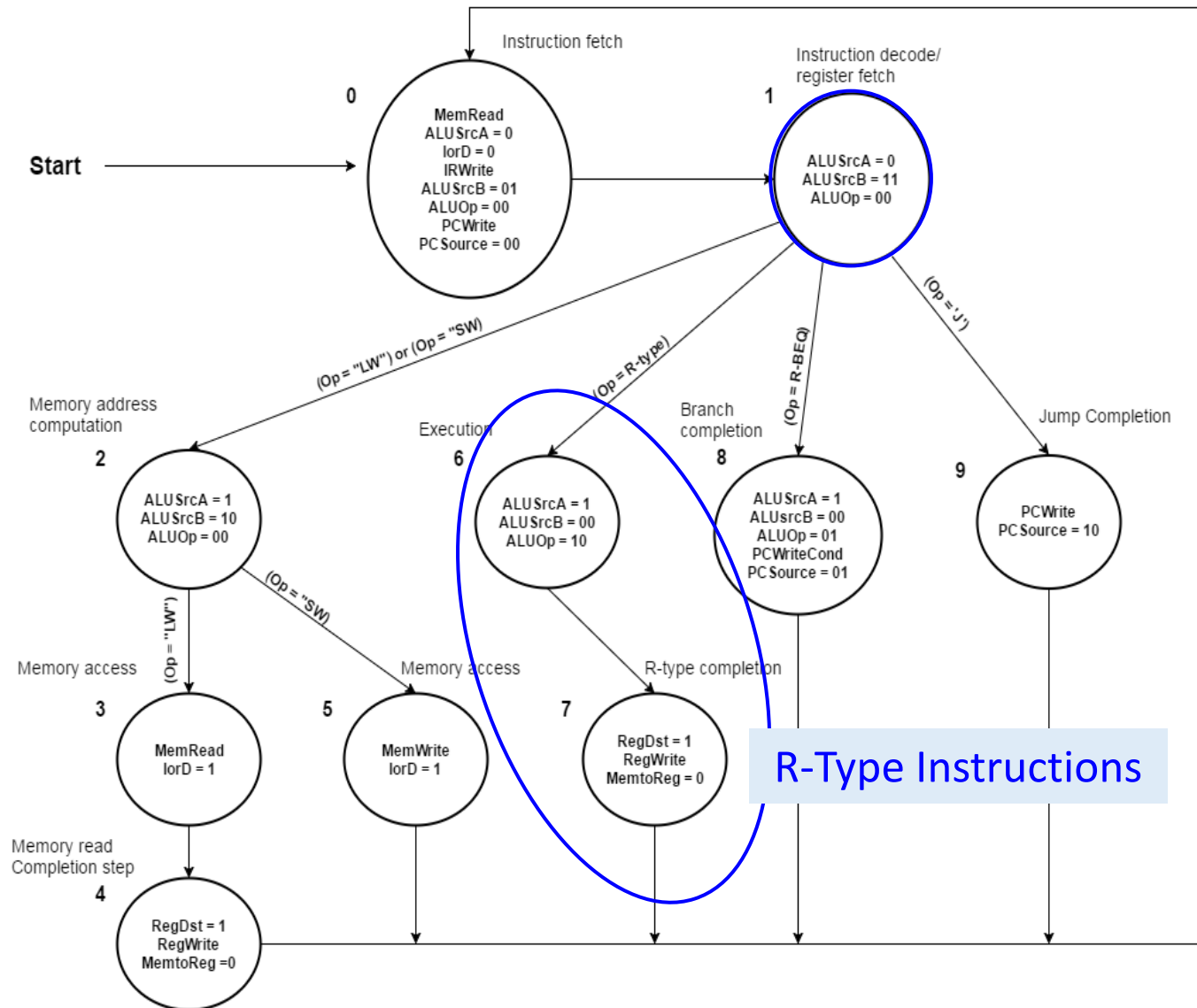Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed



R-Type Instruction Format

31-26	25-21	20-16	15-11	10-6	5-0
<i>opcode</i> (000000)	<i>rs</i>	<i>rt</i>	<i>rd</i>	<i>shamt</i>	<i>funct</i>

- ***rs*** and ***rt*** are operand registers; ***rd*** is the destination register.
- **R-Type**: Register-based ALU operations.
- ***opcode*** is always 000000.
- The actual instruction code is in the ***funct*** field (5-0).
- ***shamt*** is the “shift amount” for shift instructions.
- MIPS-4712 R-type instructions: (See MIPS instruction Set Manual for details):
add, addu, and, mfhi, mflo, mult, multu, or, sll, sltu, sra, srl, sub, subu, xor
- Example: `and $s4, $s2, $s3` (`s4 = s2 and s3`) or (`reg20 = reg18 and reg19`)
000000 10010 10011 10100 00000 100100


I-Type Instruction Format (ALU immediate)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>immed.</i>

- ***rs*** is operand A register and ***rt*** is destination register.
- ***immed.*** is operand B.
- MIPS-4712 I-type ALU insts.: *addiu, andi, ori, “subiu” (does not exist), xori*
- Example: `addiu $s2, $s1, 7` (`s2 = s1 + 7`) or (`reg18 = reg17 + 7`)
001100 10011 01010 000000000000111

Figure 3. General algorithm for designing a controller for a MIPS CPU

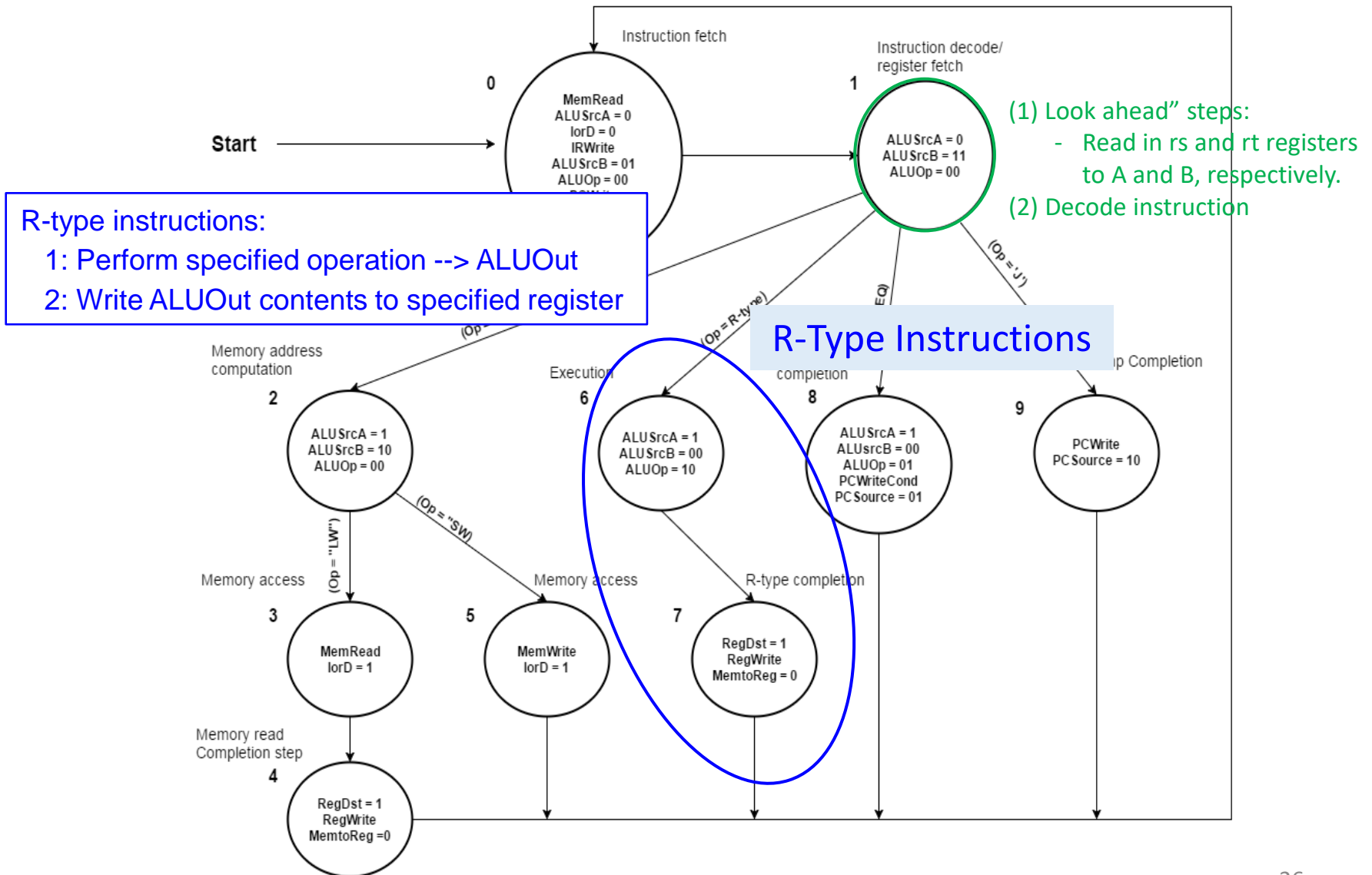Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed




R-type instructions:

1: Perform specified operation --> ALUOut


2: Write ALUOut contents to specified register

Execution of R-type instructions

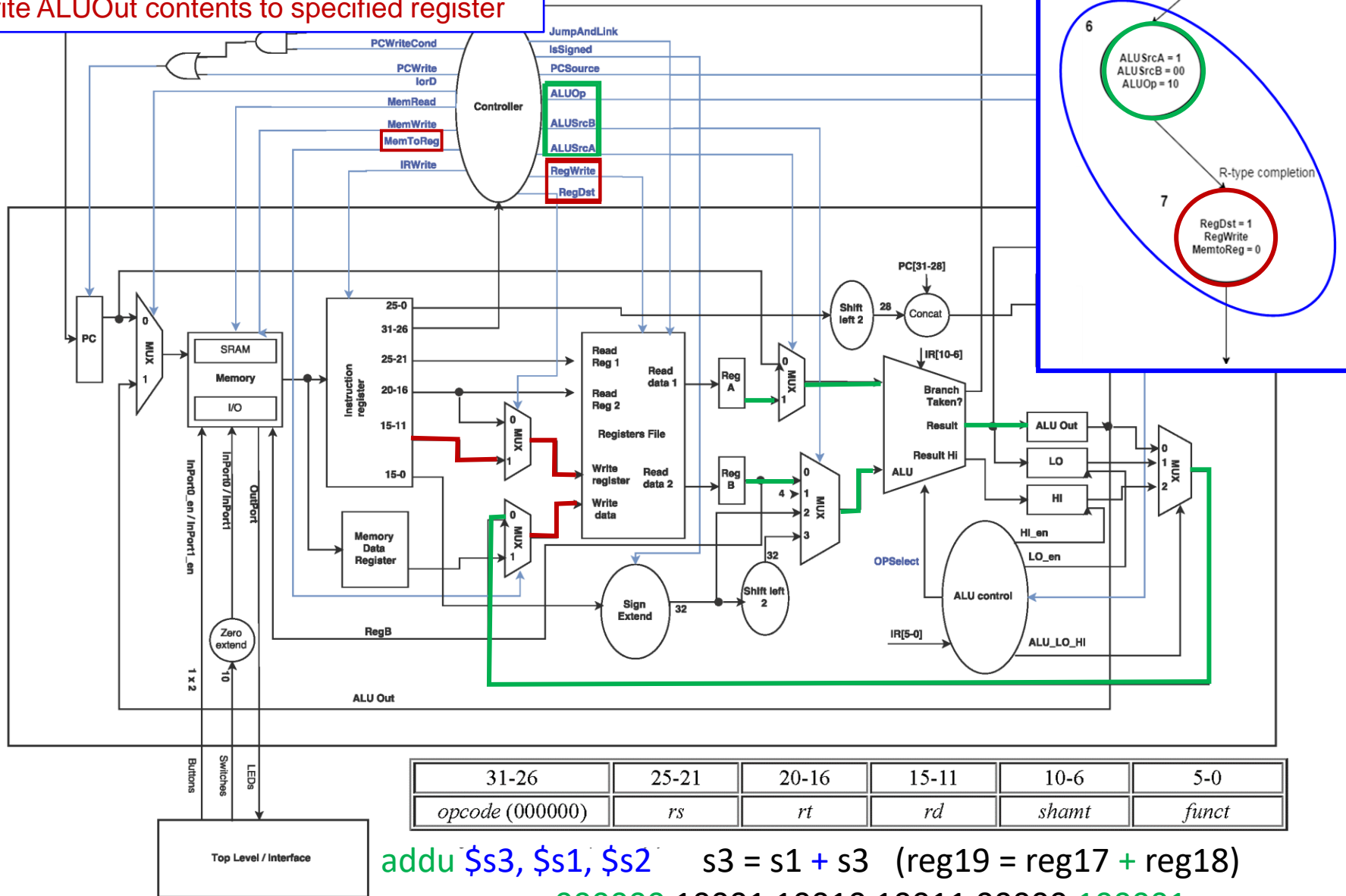

ALU Control Unit

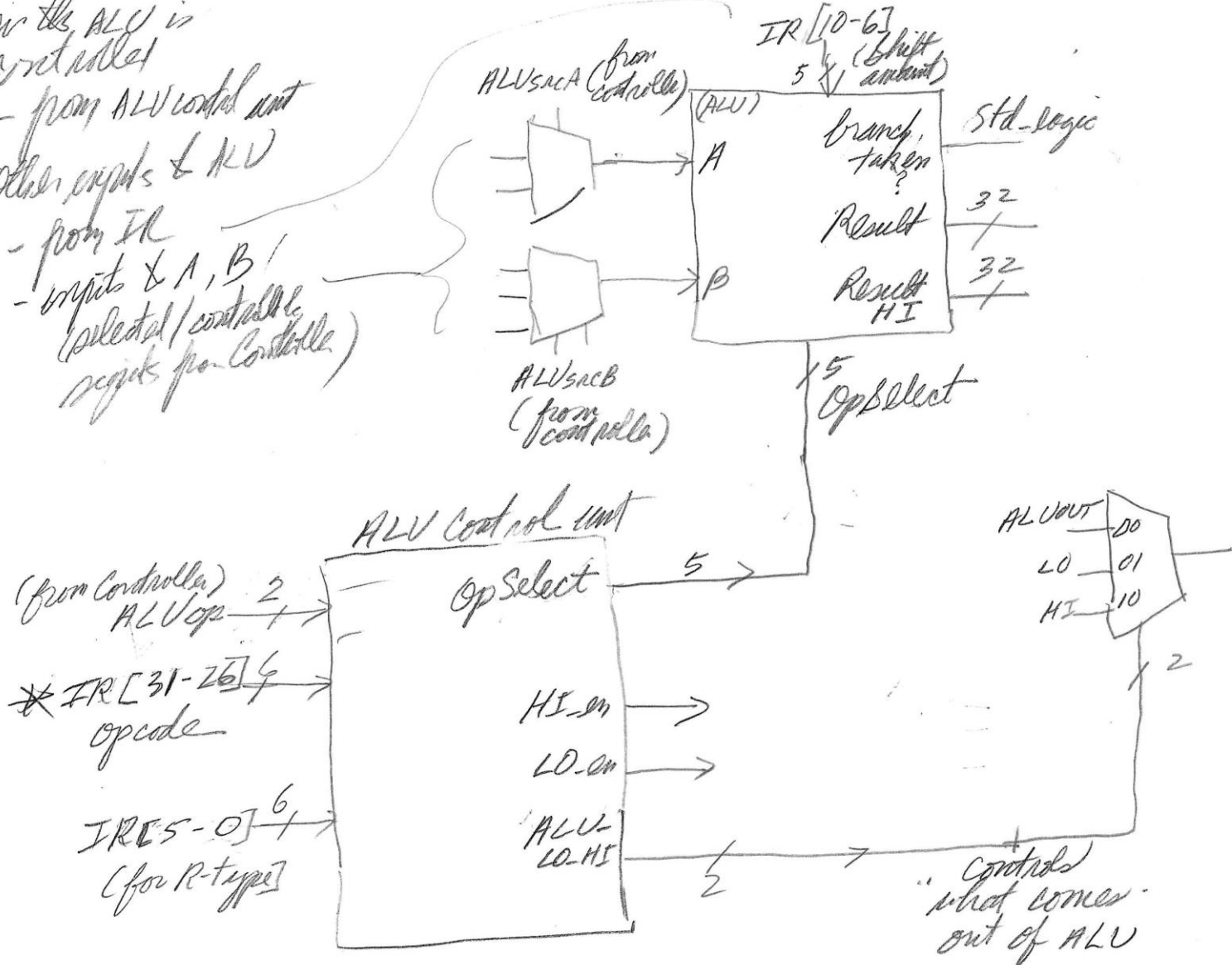- How the ALU is controlled
 - from ALU control unit
- Other inputs to ALU
 - from IR
 - inputs to A, B (selected/controllable signals from Controller)



* Not in Figure 2 (General architecture of MIPS CPU)

ALU Control Unit ("algorithm" for OpSelect output)

IF $ALUOp = 00$ (for State 0 (fetch), State 1 (decode), State 2)

$ALU.OpSelect \rightarrow "add"$

ELSEIF $ALUOp = 10$ (State 6 R-type)

CASE $IR[5-0]$ (for the actual operation)

WHEN "100001"

$ALU.OpSelect \rightarrow "addu"$

WHEN "100011"

$ALU.OpSelect \rightarrow "subu"$

⋮

etc. for all R-type instructions

ELSE (for all the other instructions using opcode field)

CASE $IR[31-26]$ (Opcode in IR register)

WHEN "001001"

$ALU.OpSelect \rightarrow "addiu"$

WHEN "001100"

$ALU.OpSelect \rightarrow "andi"$

⋮


WHEN "etc"

$ALU.OpSelect \rightarrow "etc."$

other I-type
branch

Figure 3. General algorithm for designing a controller for a MIPS CPU

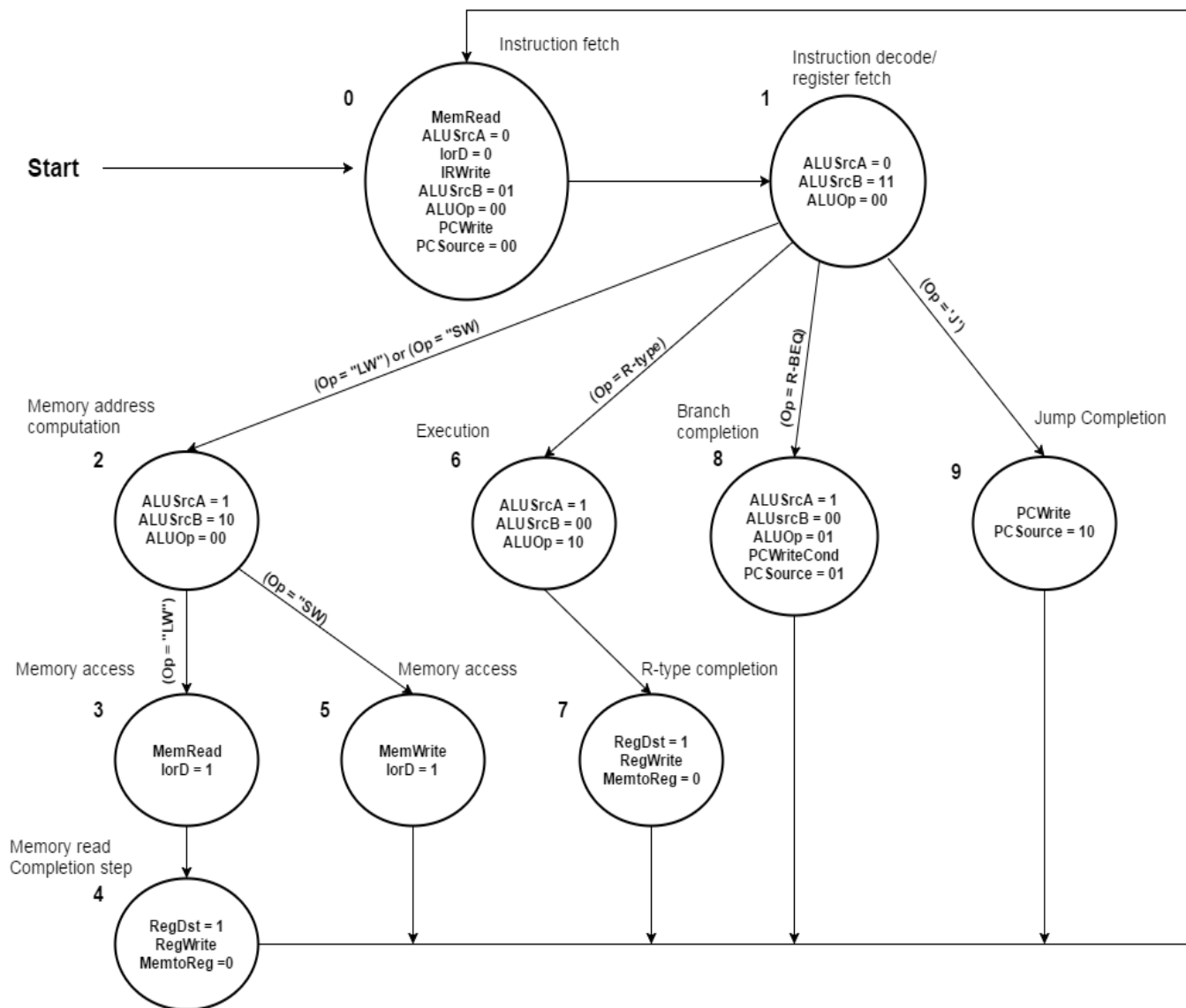Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed



Upcoming Lectures

- Go over Testcase1.mif
 - Discuss each assembly instruction and the results (in memory or registers)
- Use Testcase 1 to demonstrate the tutorial on how to view RAM and Register File contents in ModelSim:
 - Start from “scratch” and create new ModelSim project, include all .vhd files, compile, simulate
 - Follow tutorial to show contents of RAM and Register File using Testcase 1.
- Demonstrate how to see signals of internal components in the Wave window. For example:
 - Cannot see “LO” register using tutorial for Testcase1.mif.
 - If simulation is incorrect in some of the instructions, may want to “trace” through the content of a register when each instruction is being executed.
- Go through rest of the testcases:
 - Testcase2.mif
 - Testcase4.mif
 - Testcase7.mif
 - Deliverable4.mif
- Assemble GCD assembly code to machine code
- Branch (BEQ, BNE) implementation
- Discuss the implementation (not illustrate in detail like before) of:
 - J and JAL instructions (TestCase7)
 - Other instructions in TestCase7 (lw and sw to ports)

TestCase7.mif (MIPS assembly code to machine code)

00 : 00001100000000000000000000000010; -- jal 2 / jump to address 2; \$ra/r31 = 4
 01 : 00001000000000000000000000000001; -- j 1 / infinite loop
 02 : 000000000000000001000100000100001; -- addu \$s1, \$zero, \$zero
 03 : 100011100011001000000000000101000; -- lw \$s2, 0A(\$s1)
 04 : 00010010010000000000000000000011; -- beq \$s2, \$zero, 8
 05 : 001001100011000100000000000000100; -- addiu \$s1, \$s1, 4
 06 : 00000010011100101001100000100001; -- addu \$s3, \$s3, \$s2
 07 : 00001000000000000000000000000011; -- j 3
 08 : 10101100000100111111111111111100; -- sw \$s3, FFFC(\$zero)
 09 : 00000011111000000000000000001000; -- jr \$ra
 0A : 00000000000000000000000000000001; -- 1
 0B : ... etc. data

R-Type Instruction Format

31-26	25-21	20-16	15-11	10-6	5-0
<i>opcode</i> (000000)	<i>rs</i>	<i>rt</i>	<i>rd</i>	<i>shamt</i>	<i>funct</i>

I-Type Instruction Format (Load or Store)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>address</i>

I-Type Instruction Format (Branch)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>address</i>

J-Type Instruction Format (Jump)

31-26	25-0
<i>opcode</i>	<i>target</i>

Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed


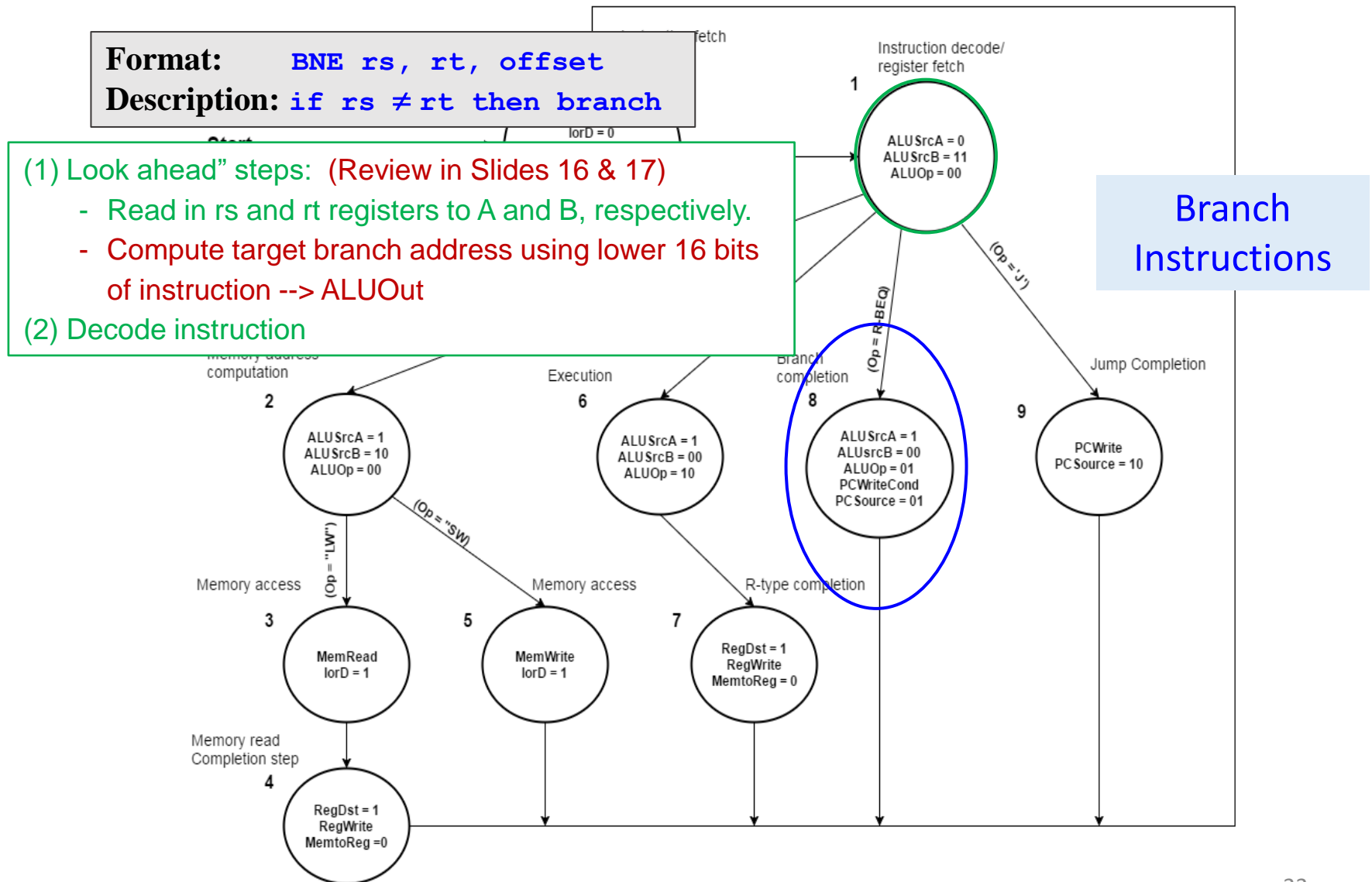


Illustration of a branch (e.g., bne) instruction

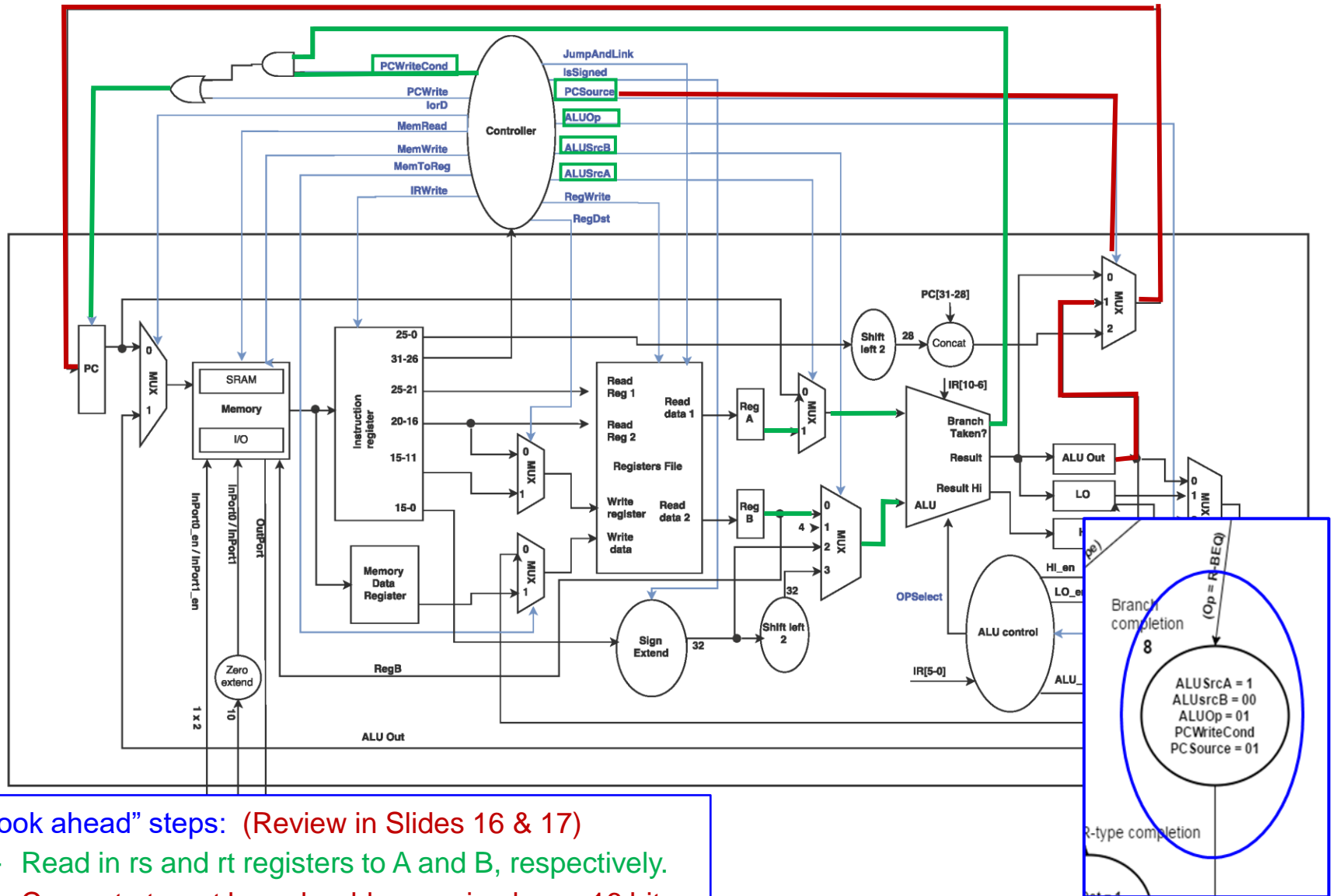

(1) Look ahead" steps: (Review in Slides 16 & 17)

- Read in *rs* and *rt* registers to A and B, respectively.
- Compute target branch address using lower 16 bits of instruction --> ALUOut

(2) Decode instruction

Format: BNE *rs*, *rt*, offset
Description: if *rs* \neq *rt* then branch

Upcoming Lectures

- Go over Testcase1.mif
 - Discuss each assembly instruction and the results (in memory or registers)
- Use Testcase 1 to demonstrate the tutorial on how to view RAM and Register File contents in ModelSim:
 - Start from “scratch” and create new ModelSim project, include all .vhd files, compile, simulate
 - Follow tutorial to show contents of RAM and Register File using Testcase 1.
- Demonstrate how to see signals of internal components in the Wave window. For example:
 - Cannot see “LO” register using tutorial for Testcase1.mif.
 - If simulation is incorrect in some of the instructions, may want to “trace” through the content of a register when each instruction is being executed.
- Go through rest of the testcases:
 - Testcase2.mif
 - Testcase4.mif
 - Testcase7.mif
 - Deliverable4.mif
- Assemble GCD assembly code to machine code
- Branch (BEQ, BNE) implementation
- Discuss the implementation (not illustrate in detail like before) of:
 - JAL and JR instructions (TestCase7) – see MIPS manual.
 - Other instructions in TestCase7 (lw and sw to ports)